

# HW1

## 記憶體積體電路 Memory Circuit Design

電機 4A 109501201 陳緯亭

October 24, 2023

### 1. DC Analysis-An Invertor

(a) Plot the transfer curve in function of the  $V_{input}$  as x axle against  $V_{output}$  as y axle with  $V_{dd} = 1V$  and different ratios of  $W_p/W_n$ , such as 0.5, 1 and 2.

Table 1: The settings of  $W_p$  and  $W_n$

Node	$W_p/W_n$	$W_p(\mu m)$	$W_n(\mu m)$
ratio05	0.5	0.5	1
ratio1	1	1	1
ratio2	2	1	0.5

 


Fig. 1: Beta ratio effects

According to the Fig. 1, the transition is from high to low. When  $W_p/W_n = 1$ , the curve can be going through the center where this point here is  $V_{dd}/2$ . When  $W_p/W_n > 1$ , this make the curve shift to the right. That is because the PMOS is too strong that leads to the NMOS needs large gate source voltage to match the current in the PMOS, and vice versa. When  $W_p/W_n < 1$ , this make the curve shift to the left. The conclusion is the ratio  $W_p/W_n$  is changed the transitions region shifts.

(b) Plot the transfer curve in function of the  $V_{input}$  as x axle against  $V_{output}$  as y axle with different values of  $V_{dd} = 1$  V, 0.8 V, 0.6 V, and 0.4 V.

Table 2: The settings of  $V_{dd}$

Node	$V_{DD}$ (V)
V1	1
V08	0.8
V06	0.6
V04	0.4

For the DC operating points, the currents through the centre of the NMOS and PMOS devices must be equal and approximate to  $V_{out} = V_{dd}/2$ . The below figure indicates that these points are at about  $V_{out} = 0.5, 0.4, 0.3$ , and  $0.2$  V.

 


Fig. 2: Voltage transfer characteristics (VPC)

(c) Plot the  $I_{dd}$ , which flows from the ground to the  $V_{dd}$ , in function of the  $V_{input}$ . You may sweep the  $V_{input}$  from 0V to  $V_{dd}$  to collect the data of  $I_{dd}$  and plot it.

Table 3: The settings of  $W_p$  and  $W_n$

Signal Name	$W_p/W_n$	$W_p(\mu\text{m})$	$W_n(\mu\text{m})$
xinv05.i(mp)	0.5	0.5	1
xinv1.i(mp)	1	1	1
xinv2.i(mp)	2	1	0.5

According to Fig 3, this demonstrates that when  $V_{in} = 0$  or  $V_{in} = V_{dd}$ , the pmos is switched off. No current flows in this area. A peak current is reached, which leads to the maximum current drawn from the supply. However, the direction of  $I_{dd}$  is opposite

to the direction of the supply to ground. Therefore, the diagram is inverted.

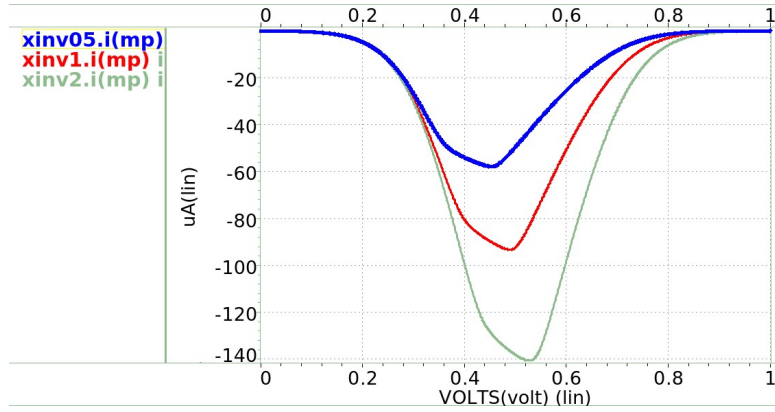


Fig. 3: The current drawn from the ground

(d) Plot the output power, which is defined as  $P_{output} = V_{output} \times I_{dd}$ . You may sweep the  $V_{input}$  from 0V to  $V_{dd}$  to collect the data of  $I_{dd}$  and  $V_{output}$ .

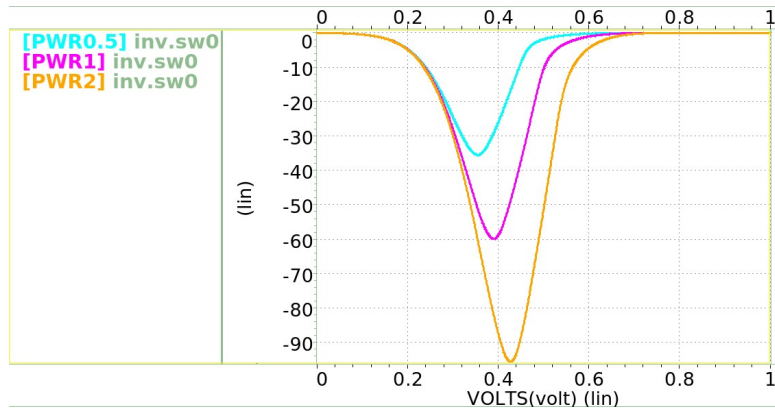


Fig. 4: DC Analysis -  $P_{output}$

Table 4: The settings of  $W_p$  and  $W_n$

Signal Name	$W_p/W_n$	$W_p(\mu\text{m})$	$W_n(\mu\text{m})$
PWR0.5	0.5	0.5	1
PWR1	1	1	1
PWR2	2	1	0.5

Mixed-Signal Equation Builder				
<input checked="" type="checkbox"/>	Name	Equation (click here to edit min/max)	Target	
<input type="checkbox"/>	PWR0.5	'i(xinv05.mp)*v(ratio05)'	D0/inv.sw0	<input type="text" value="="/>
<input type="checkbox"/>	PWR1	'i(xinv1.mp)*v(ratio1)'	D0/inv.sw0	<input type="text" value="="/>
<input type="checkbox"/>	PWR2	'i(xinv2.mp)*v(ratio2)'	D0/inv.sw0	<input type="text" value="="/>

Fig. 5: The power consumption calculated by the equation builder

## 2. Functionality of the Basic Gate

Please verify the functionality of the 2-to-1 NAND, NOR, XOR.

- NAND

Table 5: 4 output results of NAND

vain	vbin	vout
0	0	1
0	1	1
1	0	1
1	1	0

There are two kinds of input  $v_{ain}$  and  $v_{bin}$ . This means that there are 4 output results which shown in Table 5.

 


Fig. 6: 4T Nand Gate

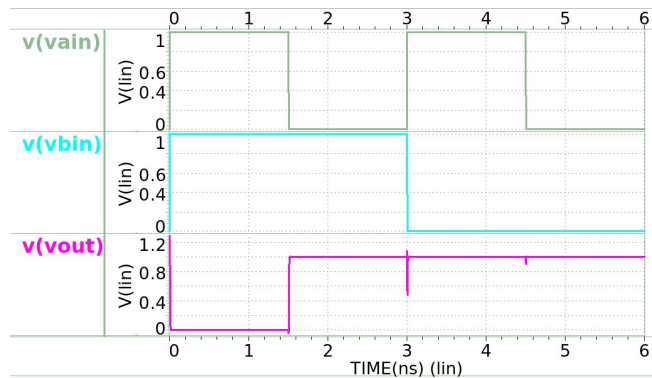


Fig. 7: Waveform for NAND's functionality

- NOR

Table 6: 4 output results of NOR

vain	vbin	vout
0	0	1
0	1	0
1	0	0
1	1	0

There are two kinds of input  $v_{ain}$  and  $v_{bin}$ . This means that there are 4 output results which shown in Table 6.

 


Fig. 8: 4T NOR Gate

 


Fig. 9: Waveform for NOR's functionality

- XOR

Table 7: 4 output results of XOR

a	b	vout
0	0	0
0	1	1
1	0	1
1	1	0

There are two kinds of input  $a$  and  $b$ . This means that there are 4 output results which shown in Table 7.

 


Fig. 10: 12T XOR Gate

 


Fig. 11: Waveform for XOR's functionality

### 3. Functionality of the Transmission Gate

Please verify the functionality of transmission gate.

Table 8: 4 output results of TG

en	vin	vout
1	0	0
1	1	1
0	0	High impedance or floating
0	1	High impedance or floating

There are two kinds of input  $vin$  and  $en$ . This means that there are 4 output results which shown in Table 8.

 


Fig. 12: 4T Transmission Gate

 


Fig. 13: Waveform for TG's functionality

### 4. Functionality of the Basic Gate

Please verify the functionality of the 4-to-1 MUX.

There are two kinds of main control signal  $s_0$  and  $s_1$ . The result is shown in Fig. 8.

Table 9: 4 output results of 4-to-1 MUX

$s_1$	$s_0$	vout
0	0	d0
0	1	d1
1	0	d2
1	1	d3

 


Fig. 14: 14T 4-to-1 MUX

 


Fig. 15: Waveform for 4-to-1 MUX's functionality

## 5. Functionality of the Decoder

Please verify the functionality of the 3-to-8 decoder.

Table 10: 9 output results of 3-to-8 Decoder

<i>en</i>	<i>c</i>	<i>b</i>	<i>a</i>	<i>d0</i>	<i>d1</i>	<i>d2</i>	<i>d3</i>	<i>d4</i>	<i>d5</i>	<i>d6</i>	<i>d7</i>
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

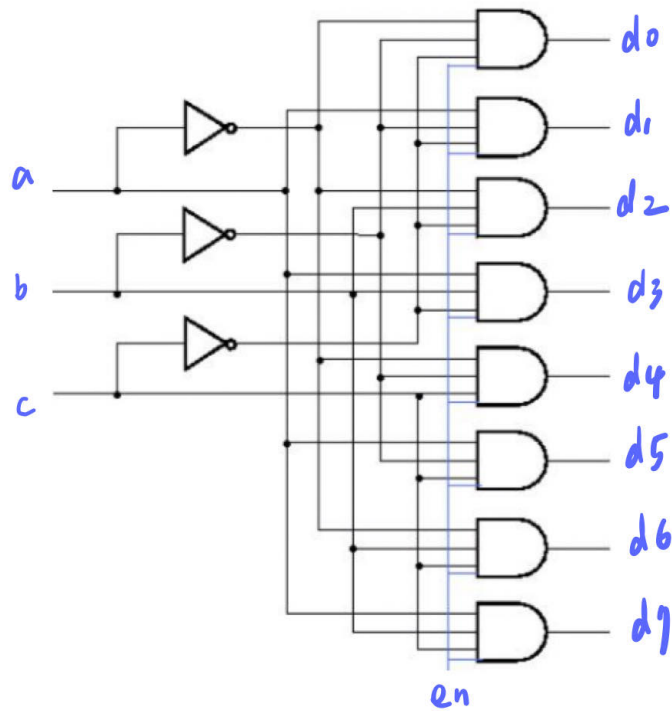


Fig. 16: 86T 3-to-8 decoder

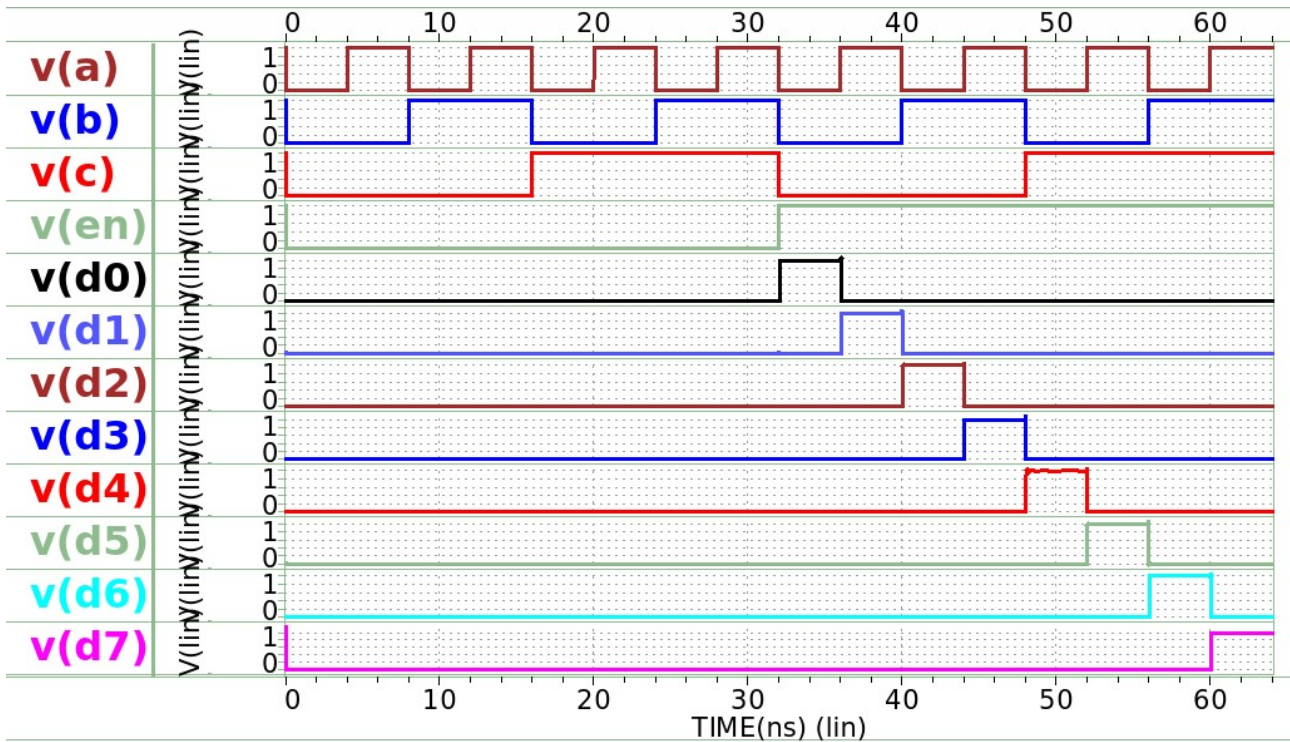


Fig. 17: Waveform for 3-to-8 decoder's functionality